

ECE 145C / 218C, notes set xx: g_m - Z_t Amplifiers

Mark Rodwell

Doluca Family chair

University of California, Santa Barbara

We must often design broadband gain blocks

Baseband amplifiers for high-data-rate wireless


Also for

....optical fiber receivers

....and "wireline" (electrical wire) interfaces


Symbol rates can exceed 100 Gbaud

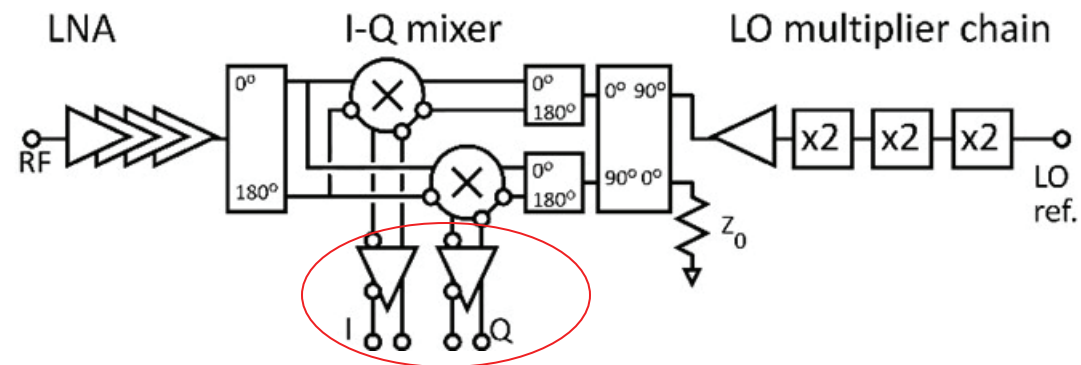...resistive feedback amplifiers and g_m - Z_t amplifiers are useful for these



Transconductance Blocks

Basic transconductance blocks

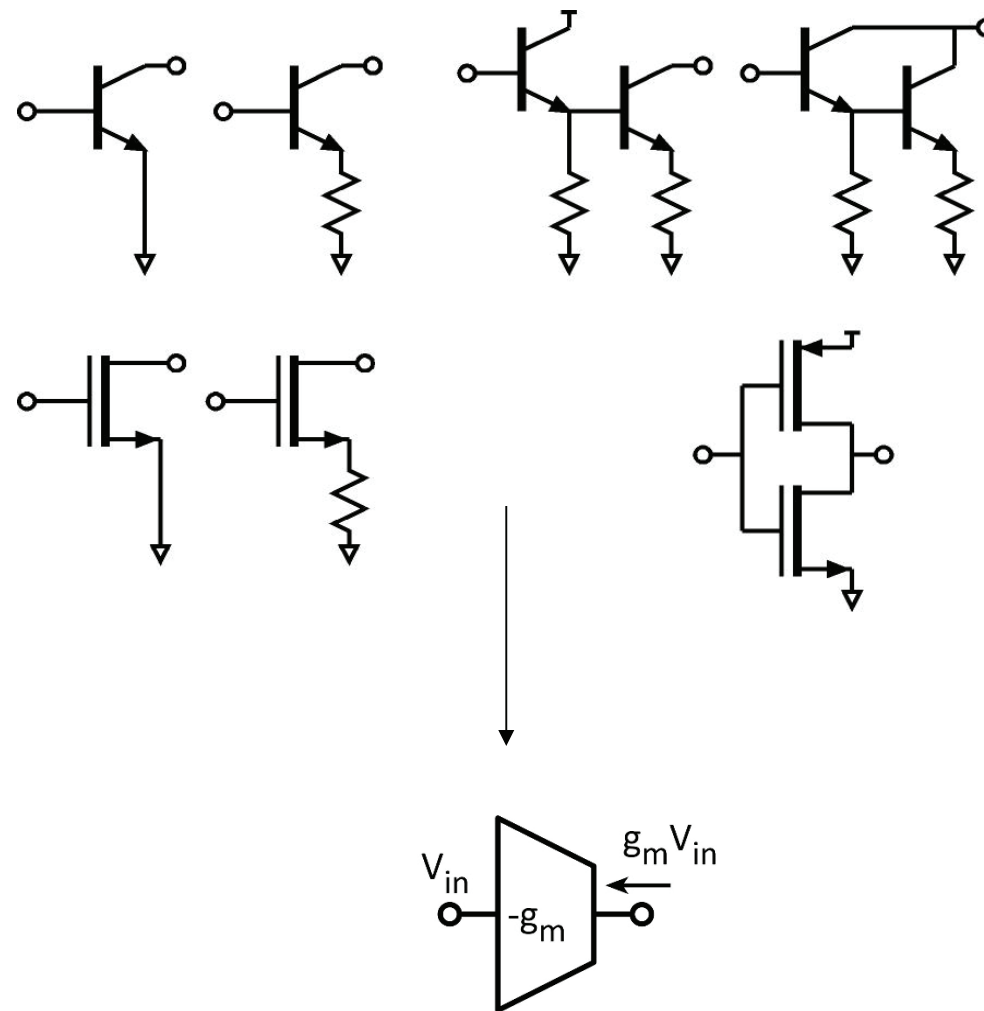

Simple Transconductance Block Model

Simple FET model, neglecting $R_g, R_{DS}, R_s \dots$

Capacitances are proportional to W_g

g_m is proportional to W_g




\Rightarrow Capacitances are proportional to g_m

$$C_{in} = \tau_{in} g_m$$

$$C_{out} = \tau_{out} g_m$$

$$C_f = \tau_f g_m$$
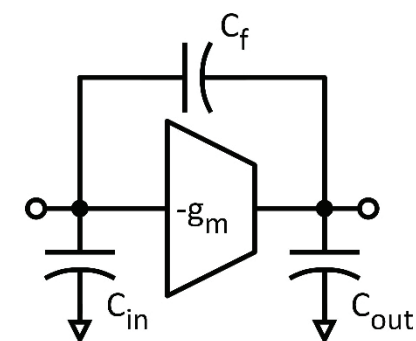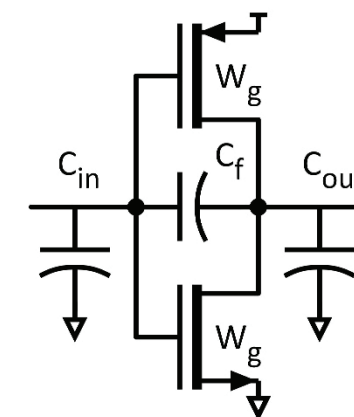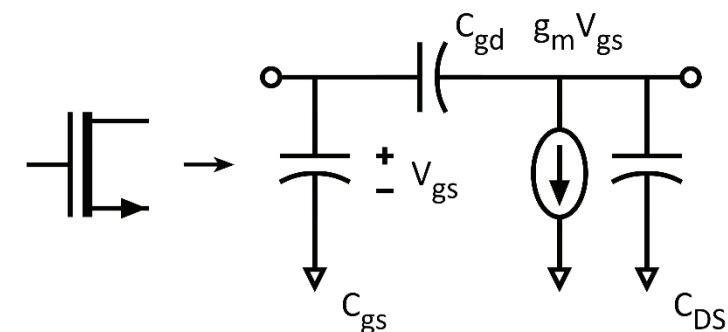
$$\frac{1}{2\pi f_\tau} = \tau_{in} + \tau_f$$



Transimpedance Block

Transimpedance block:

$$I_{out} = -I_{in} \rightarrow V_{in} = I_{in} / g_m$$

$$V_{in} - V_{out} = I_{in} R_f$$

$$\rightarrow V_{out} = Z_T I_{in} \text{ where } Z_T = -(R_f - g_m^{-1})$$



$$\rightarrow R_{in} = 1 / g_m$$

Output resistance:



$$I_{out} = I_{test} \rightarrow V_{in} = I_{test} / g_m$$

$$V_{in} - V_{out} = 0 \text{ Volts (no current in } R_f)$$
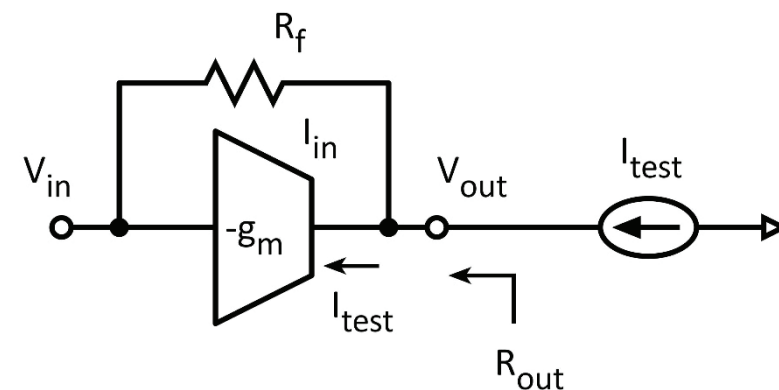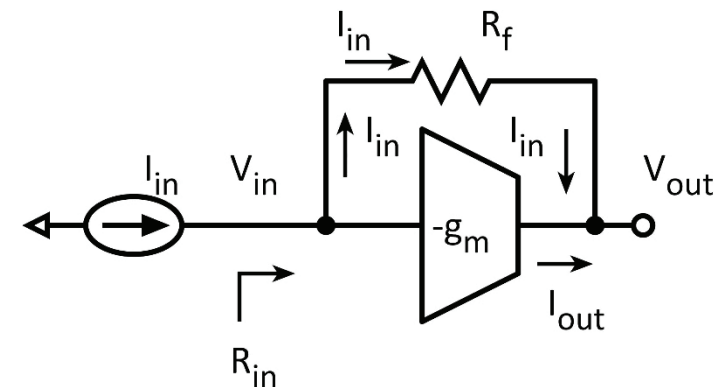
$$\rightarrow V_{out} = R_{out} I_{test} \text{ where } R_{out} = 1 / g_m$$





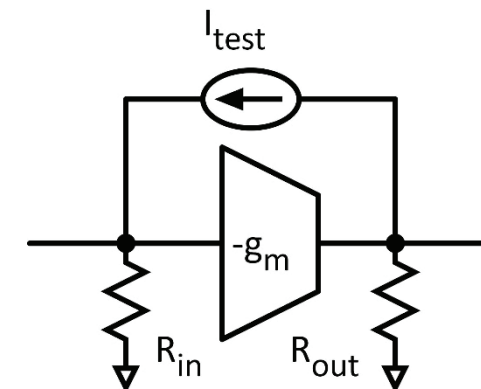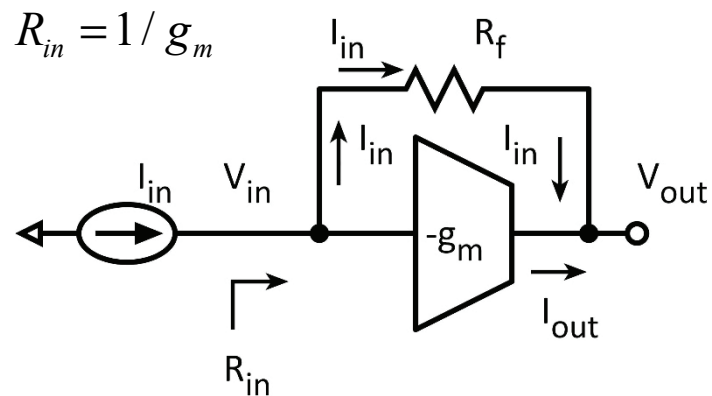Transimpedance Block: MOTC Port Resistances



$$V_{test} / I_{test} = R_{xx}^0 = R_{in} (1 + g_m R_{out}) + R_{out}$$

$$R_{out} = 1 / g_m$$

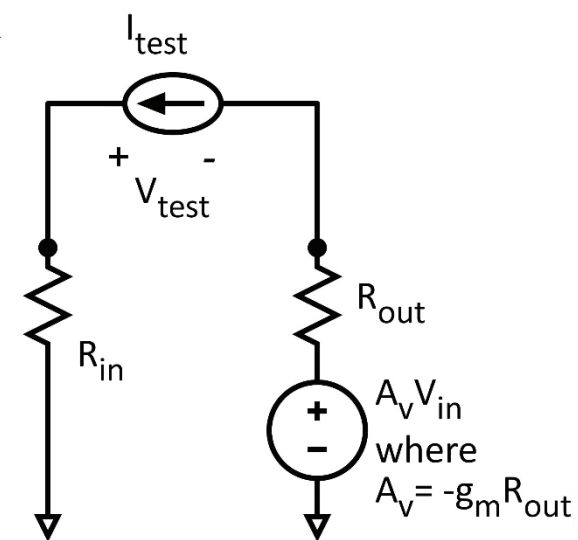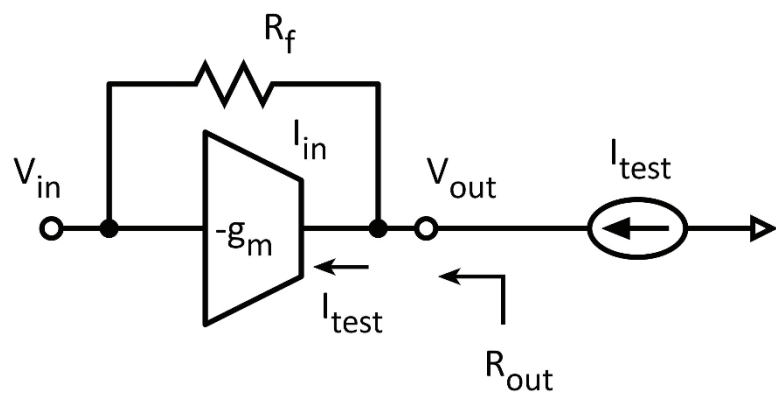


Transconductance-Transimpedance Amplifier



$$V_{out} = -(R_f - g_{m2}^{-1})I_{in2}$$

$$\text{but } I_{in2} = -g_{m1}V_{in}$$
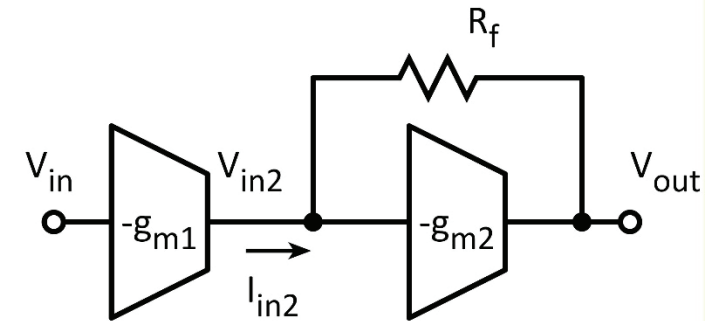
$$\rightarrow V_{out} = g_{m1}Z_T V_{in} \text{ where } Z_T = (R_f - g_{m2}^{-1})$$



Examples:

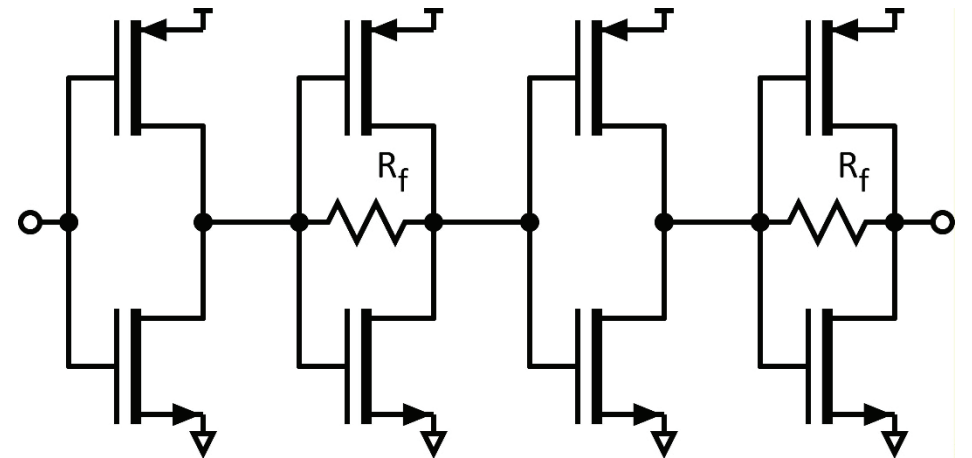
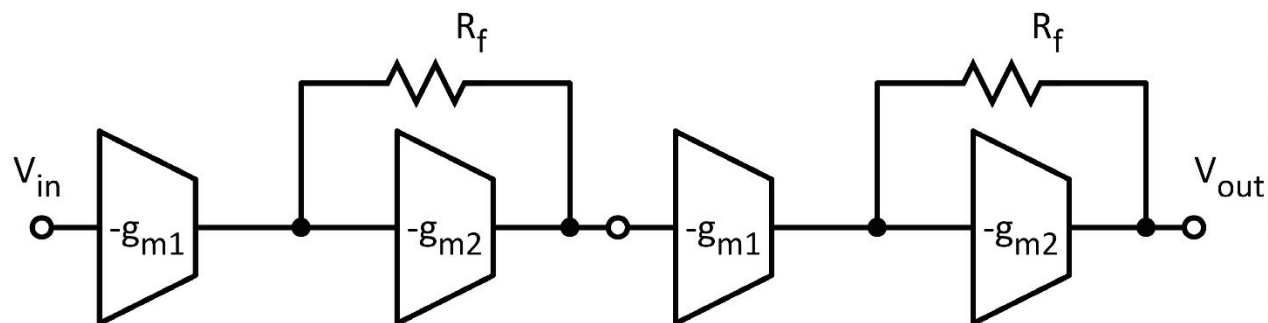


g_m - Z_t frequency response analysis (1)

In a multi-stage g_m - Z_t amplifier,
analysis cannot isolate into individual blocks
→ difficult.

Let us approximate by neglecting C_f
in the g_m (not Z_t) blocks:

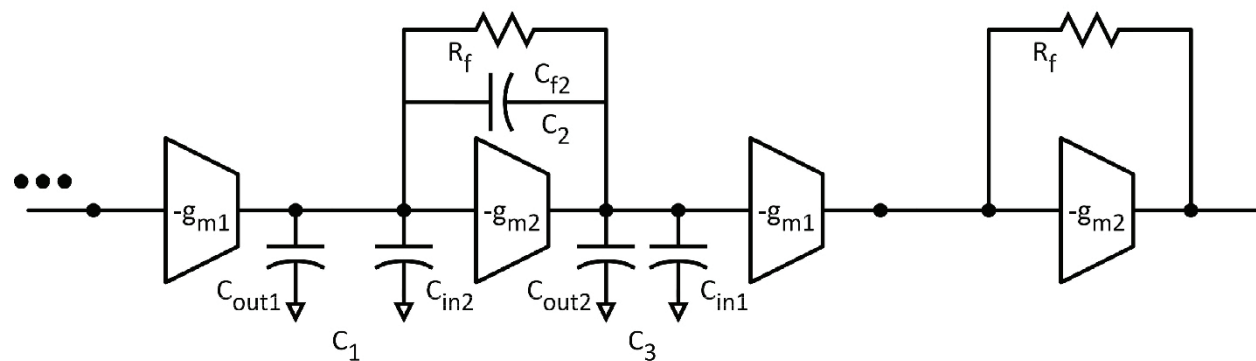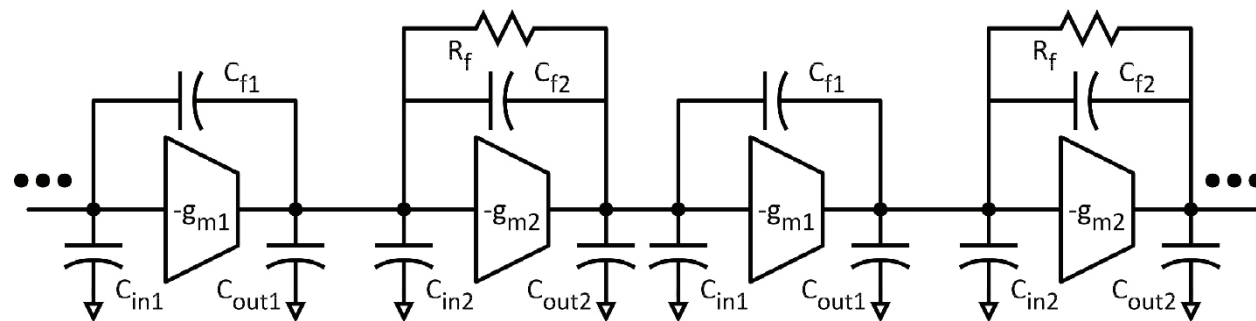This then becomes solvable to give
a per-stage transfer function



g_m - Z_t frequency response analysis (2)

$$a_1 = R_{11}^0 C_1 + R_{22}^0 C_2 + R_{33}^0 C_3 = g_{m2}^{-1} C_1 + R_f C_2 + g_{m2}^{-1} C_3$$

$$R_{22}^1 = R_f ; R_{33}^1 = R_f ; R_{33}^2 = g_{m2}^{-1}$$



$$\begin{aligned} a_2 &= R_{11}^0 C_1 R_{22}^1 C_2 + R_{11}^0 C_1 R_{33}^1 C_3 + R_{22}^0 C_2 R_{33}^2 C_3 \\ &= g_{m2}^{-1} C_1 R_f C_2 + g_{m2}^{-1} C_1 R_f C_3 + R_f C_2 g_{m2}^{-1} C_3 \\ &= g_{m2}^{-1} R_f (C_1 C_2 + C_1 C_3 + C_2 C_3) \end{aligned}$$

where $C_1 = C_{out1} + C_{in2}$, $C_2 = C_{f2}$, and $C_3 = C_{out2} + C_{in1}$

and $C_{in1} = \tau_{in} W_{g1}$, $C_{out1} = \tau_{out} W_{g1}$, $C_{in2} = \tau_{in} W_{g2}$, $C_{out2} = \tau_{out} W_{g2}$, $C_{f2} = \tau_f W_{g2}$,

Giving $\omega_n = a_2^{-1/2}$ and $\zeta = a_1 a_2^{-1/2} / 2$

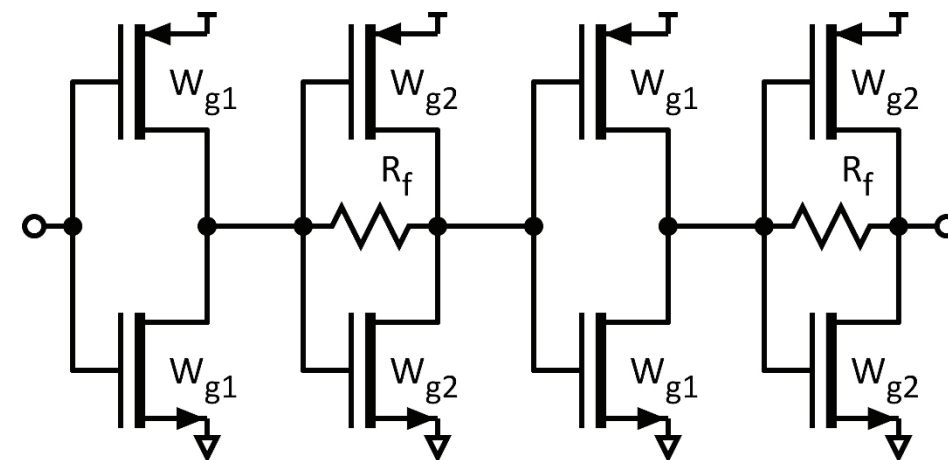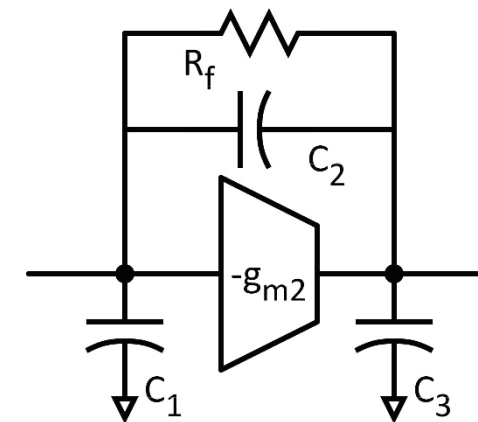We can now find the amplifier bandwidth and damping factor as a function of the selected transistor sizes



Nested loop g_m - Z_t amplifier

We synthesize an overall resistive feedback amplifier satisfying

$$g_{m4} = (1 - A_{v,overall}) / Z_o$$


$$R_{f1} = Z_o (1 - A_{v,overall})$$

So as to give (negative) gain $A_{v,overall}$ and $Z_{in} = Z_{out} = Z_o$

The overall transconductance g_{m4} is synthesized from a g_m - Z_t amplifier (g_{m1}, g_{m2}) and a transconductance block (g_{m3}).

The nested design permits a large per-state gain, hence a large R_{f1} , minimizing its noise contribution.

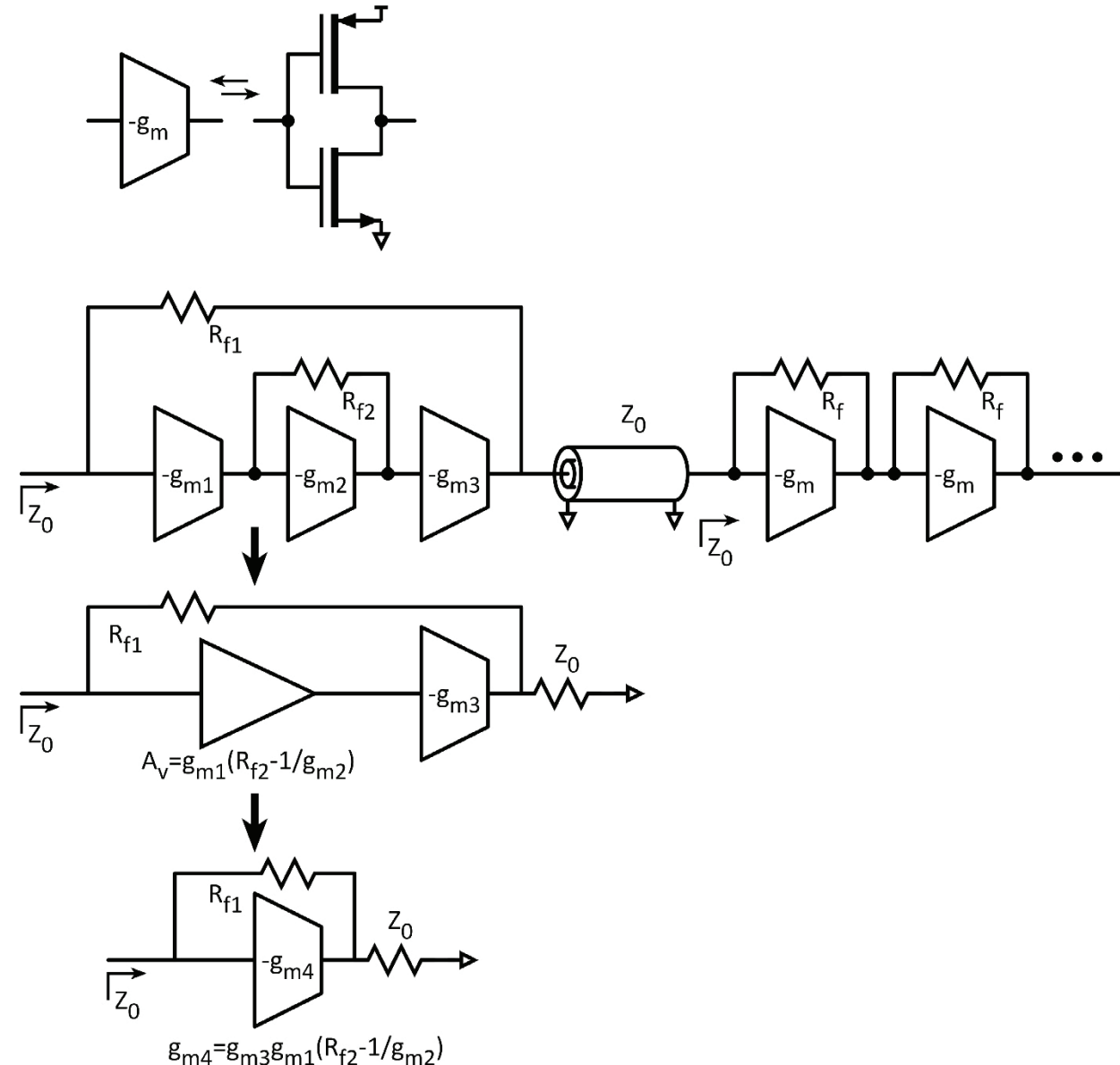Careful loop stability analysis is advised



Nested loop g_m - Z_t amplifier

Example design in 45 nm SOI CMOS.

~15 GHz bandwidth, 26 dB gain

Relatively low noise for a broadband design.

