 


**ECE 145C/218C second problem set: AGC loops**


Problem 1: You will be working with the peak detector / power detector shown to the right.  $V_{CC} = 5V$ . Pick  $R_1 + R_2$  such that  $I_{REF} = 5\text{ mA}$ . Pick  $C_1$  so that its capacitive reactance is less than 1 Ohm at 500 kHz. Let us \*initially\* pick  $R_2 = 0\text{ Ohms}$ .

First, assume that the input is a \*square wave\*.

For  $V_{pp} = 0.893\text{ Volts}$ , what value do you compute for  $V_{DET}$  ?



 Problem 2: We now simulate using a sinusoidal signal and a generator a 50 Ohm output impedance. Continue to assume a signal frequency of 500 kHz. Note that a signal generator with a 50 Ohm output impedance will deliver half the open circuit voltage to a 50 Ohm load as the inset diagram indicates;  $V_{in} = V_{GEN} / 2$ . However once we include the loading of the peak detector the input voltage  $V'_{in}$  may or may not be equal to  $V_{GEN} / 2$ .




It is however the relationship between  $V_{in}$  and  $V_{DET}$  That we are concerned about Not the relationship between  $V'_{in}$  and  $V_{DET}$ .

Using a harmonic balance simulator from ADS and sweeping the available power from the generator, with Q1 and Q2 using MRF901 transistor models, simulate the relationship between the available power from the generator and the DC voltage. Provide this graph in your homework solution

Note carefully the value of this voltage at 3 dBm available power .

Problem 3: Now, keeping the value of  $R_1 + R_2$  the same as the previous problems, Increase  $R_2$  until  $V_{DET}$  is zero when the available power from the generator is 3 dBm.

 Problem 3: You will now design and simulate a 915 MHz variable gain amplifier in ADS. Use mrf901 transistors.  $V_{CC}=5V$ . Select  $R_3$  and  $R_4$  such that the base of  $Q_1$  is biased at 2.5V and such that the current through  $R_4$  is 1 mA. Pick  $R_2$  such that it carries 5 mA. Initially simulate with  $V_{AGC}=2.0V$ . Set  $R_1=1k\Omega$ . Please initially set  $R_6 = \infty \Omega$  and  $R_5 = 0 \Omega$ ; you can choose to change these values if that makes design easier, but to do so will reduce the gain.



Design the output tuning network to provide a loadline match as this will provide the largest saturated output power. Design the input tuning network to provide a small signal match as this will provide the largest gain.

Make plots of the resulting s parameters over the frequency range from 800 to 1000 MHz. Make plots of input available power from the generator and output power delivered to a 50 Ohm load at 915 MHz signal frequency.

Problem 4: With  $V_{AGC}=2.0 V$ , the DC current in  $R_2$  will pass entirely through  $Q_1$ , with no current carried in  $Q_2$ . As  $V_{AGC}$  is increased, a greater fraction of the current will be carried in  $Q_2$ , and a lesser fraction in  $Q_1$ . This will reduce the circuit gain. The distribution of currents between the two transistors will switch very quickly as  $V_{AGC}$  is varied, with almost all of the current in  $Q_1$  for  $V_{AGC}=2.5V - 52 mV$  and with almost all of the current in  $Q_2$  for  $V_{AGC}=2.5V + 52 mV$ . This is a rapid and nonlinear variation. However the variation in gain as a function of  $I_{C1}$  will however be relatively smooth and slowly varying.

Please make a graph of the dB magnitude of S21 as a function of  $I_{C1}$ . Please also make a graph of the dB magnitude of S twenty one as a function of  $V_{AGC}$

\*\*\*\*\*

The above exercises in this problem set are to help you design the AGC loop for the receiver lab project. For your reference, the images below show some preliminary suggested signal power levels within the receiver, together with some block diagrams of what the AGC control loop might look like inclusive of the op amp feedback amplifier.

